

**Arrange circuits, control  
and  
protection  
for  
general electrical installations**

**Week 2: Fault Loop Impedance**

A QUALITY VOCATIONAL ELECTRICAL TRAINING COURSE  
PROVIDED BY: GLOBAL ENERGY TRAINING SOLUTIONS

**All writing in BLUE is examinable**

**All writing in RED  
is  
NOT examinable.**

## The cable selection process

### Glossary:

**MD = Maximum Demand**

**CB = Circuit Breaker**

**CCC = Current Carrying  
Capacity**


**VD = Voltage Drop**


**FLI = Fault Loop Impedance**

**PFC = Prospective Fault Current**

**SCTR = Short Circuit**

**Temperature Rise**

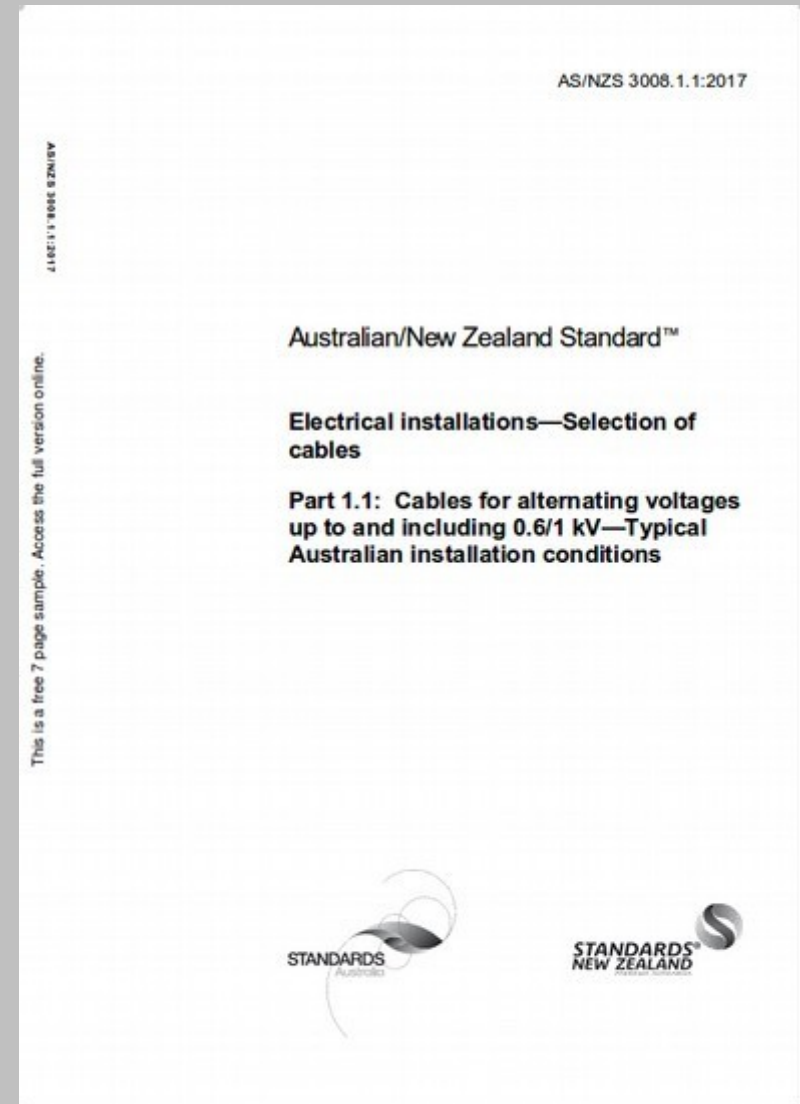

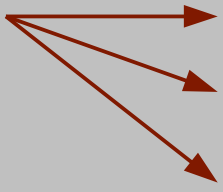1) Calculate MD (AS/NZS 3000) 

- Consumer mains (Table C1, C2, C3)
- Sub mains (Table C1, C2, C3)
- Final sub circuits (Table C4, C8)

2) Select Circuit Breaker  
(Standard sizes Table 8.1 AS/NZS 3000)

$$I_B \leq I_N \leq I_Z$$
$$MD \leq CB \leq CCC$$

2.5.3.1 AS/NZS 3000

3) Select cable based on Current Carrying Capacity  
(Table C5 and C6 AS/NZS 3000, Section 3 AS/NZS 3008)

4) Check Voltage Drop  
(3.6, Table C7 AS/NZS 3000, Section 5 AS/NZS 3008)

5) Check Fault-Loop Impedance  
(5.7, Appendix B AS/NZS 3000)

**6) Calculate Prospective Fault Current  
(2.5.4 AS/NZS 3000) However no guidance is offered in  
AS/NZS 3000**

**7) Check Short Circuit Temperature Rise  
(2.5.4 and Section 5 AS/NZS 3008)**

**This course covers FLI, SCTR and PFC, however these are  
only topics inside the much greater cable selection  
process.**

# Fault-Loop Impedance


## What you need to know about Fault-Loop Impedance

- 1) What is it?
  - Describe the loop
  - Why it is an issue
  
- 2) How to select cables so that maximum lengths are not exceeded:
  - $L_{max}$
  - Table B1
  
- 3) How to test it: (Z<sub>max</sub>)
  - Table 8.1 (live)
  - Table 8.2 (dead)
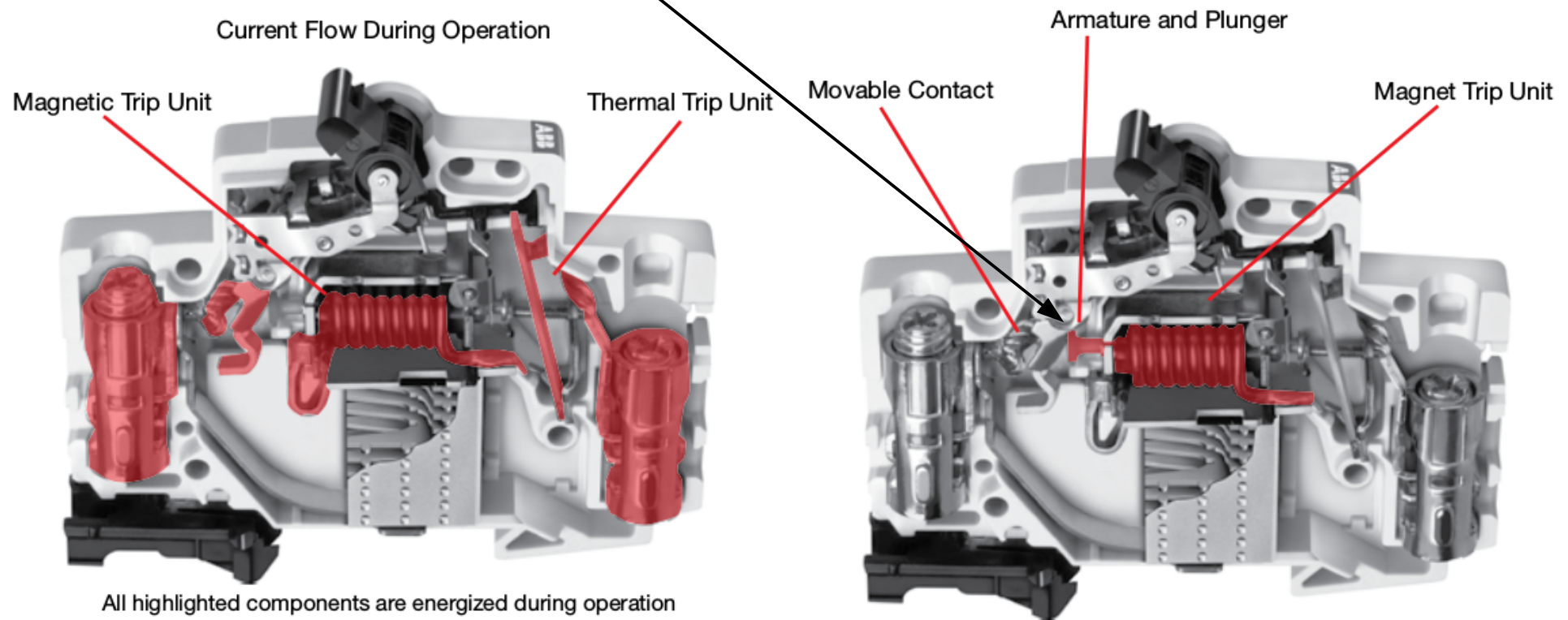
## Circuit breakers


If not enough current flows this Solenoid wont trip during a short.

We calculate this using another application of Ohms law.



Thermal trip  
(Bi-metal Strip)  
(Conventional trip  
Time)

$$(I_B \leq I_N \leq I_Z)$$

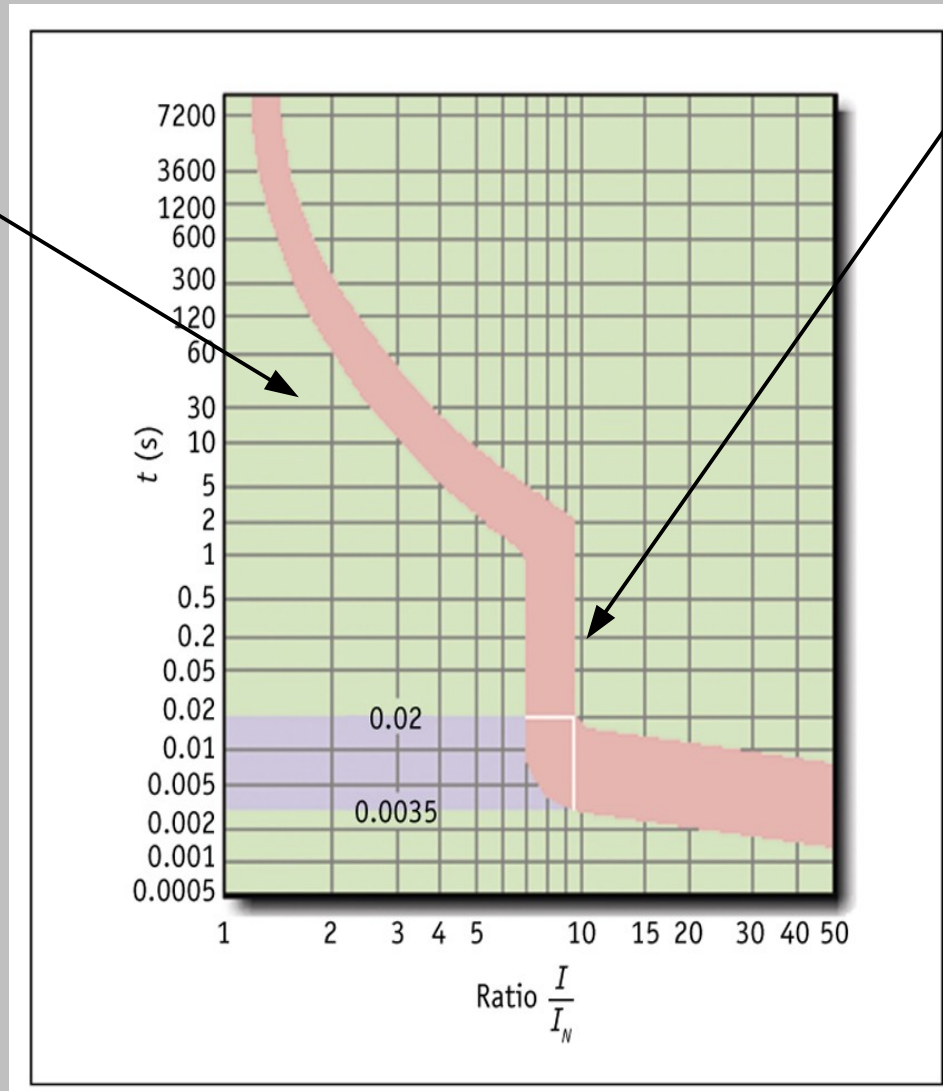

Magnetic trip  
(Solenoid)  
(Instantaneous  
Trip)  
(Fault-Loop  
Impedance)



## Not all circuit breakers trip the same

**Type B – 4 x overload  $20A \times 4 = 80A$  to trip instantly**

**Type C – 7.5 x overload  $20A \times 7.5 = 150A$  to trip instantly**

**Type D – 12.5 x overload  $20A \times 12.5 = 250A$  to trip instantly  
(B4.5 AS/NZS 3000)**


**Type B – Where a fast trip time is required  
or to protect a sensitive load**

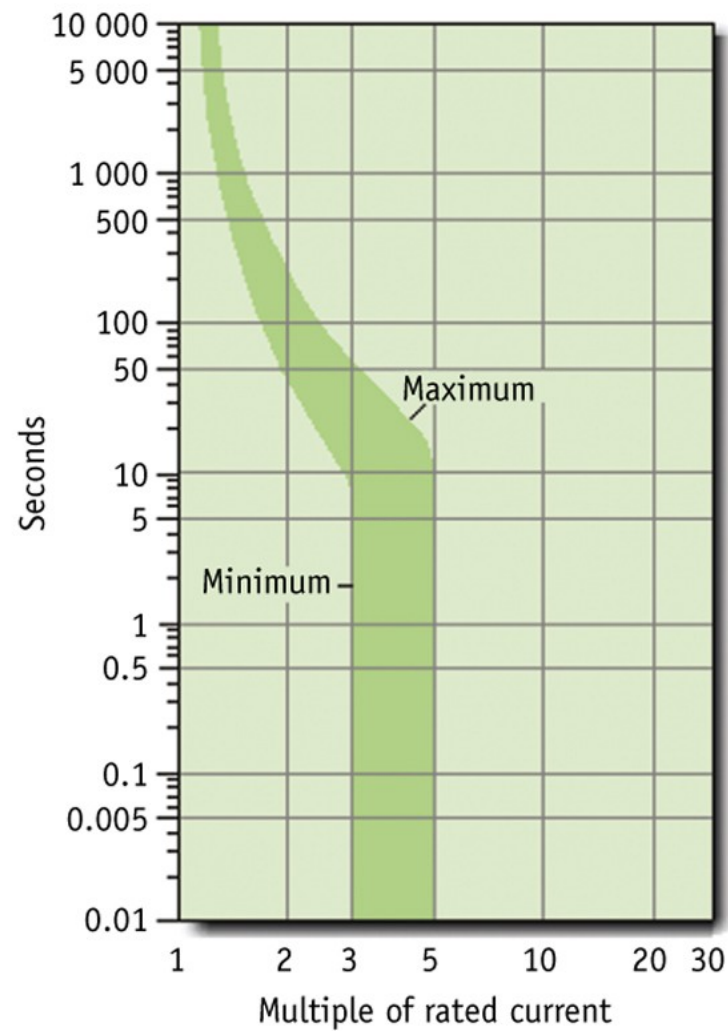**Type C – All common CB's**


**Type D – Used for high start up current  
applications such as Direct On Line (DOL)  
motors**

**The letter is indicated on CB's C20  
= Type C 20A CB**






**Type B: 4 x**

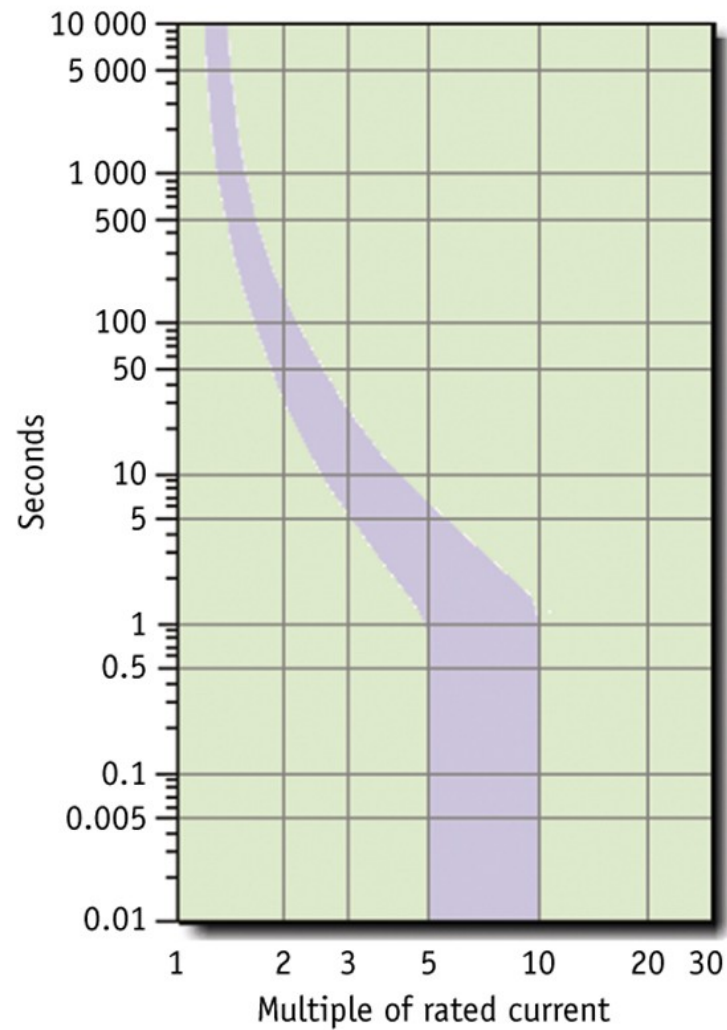

**Type C: 7.5 x**

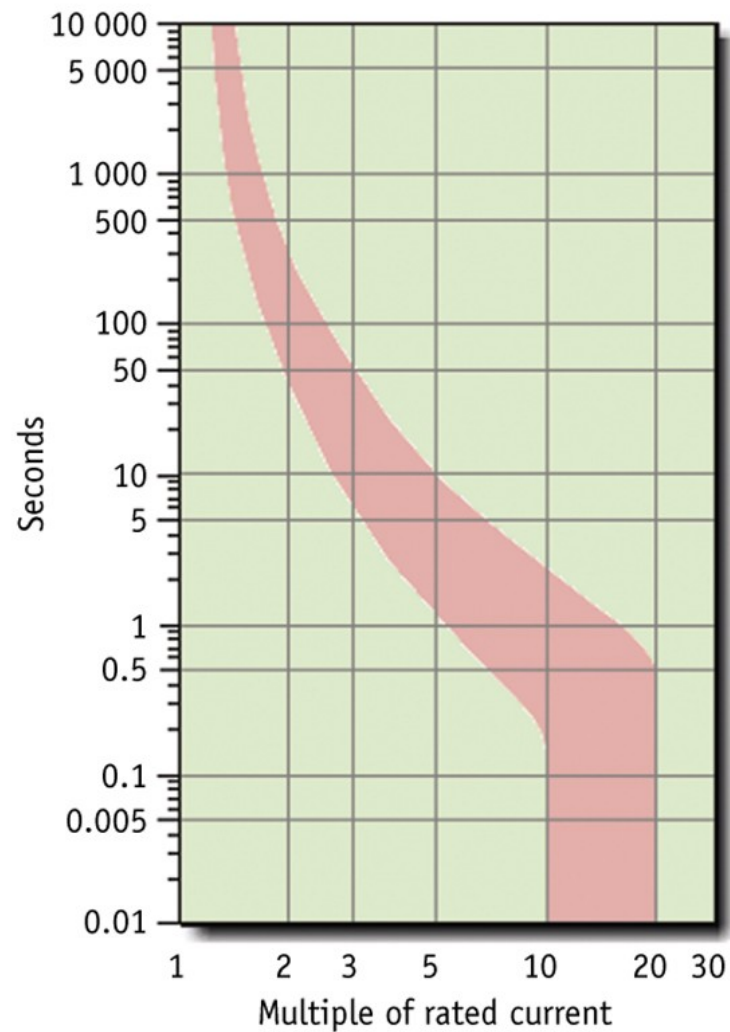

**Type D: 12.5 x**

**Glossary:**

**FLI = Fault-Loop Impedance**

**TX = Transformer**

**CM = Consumer Main**

**MSB = Main Switch Board**

**SM = Sub-Main**

**DB = Distribution Board**

**FSC = Final Sub-Circuit**

**Load = Load**


**P/E = Protective Earth**


**M/E = Main Earth**

**MEN = Main Earth Neutral**

**PEN = Protective Earth Neutral**

# The Fault Loop

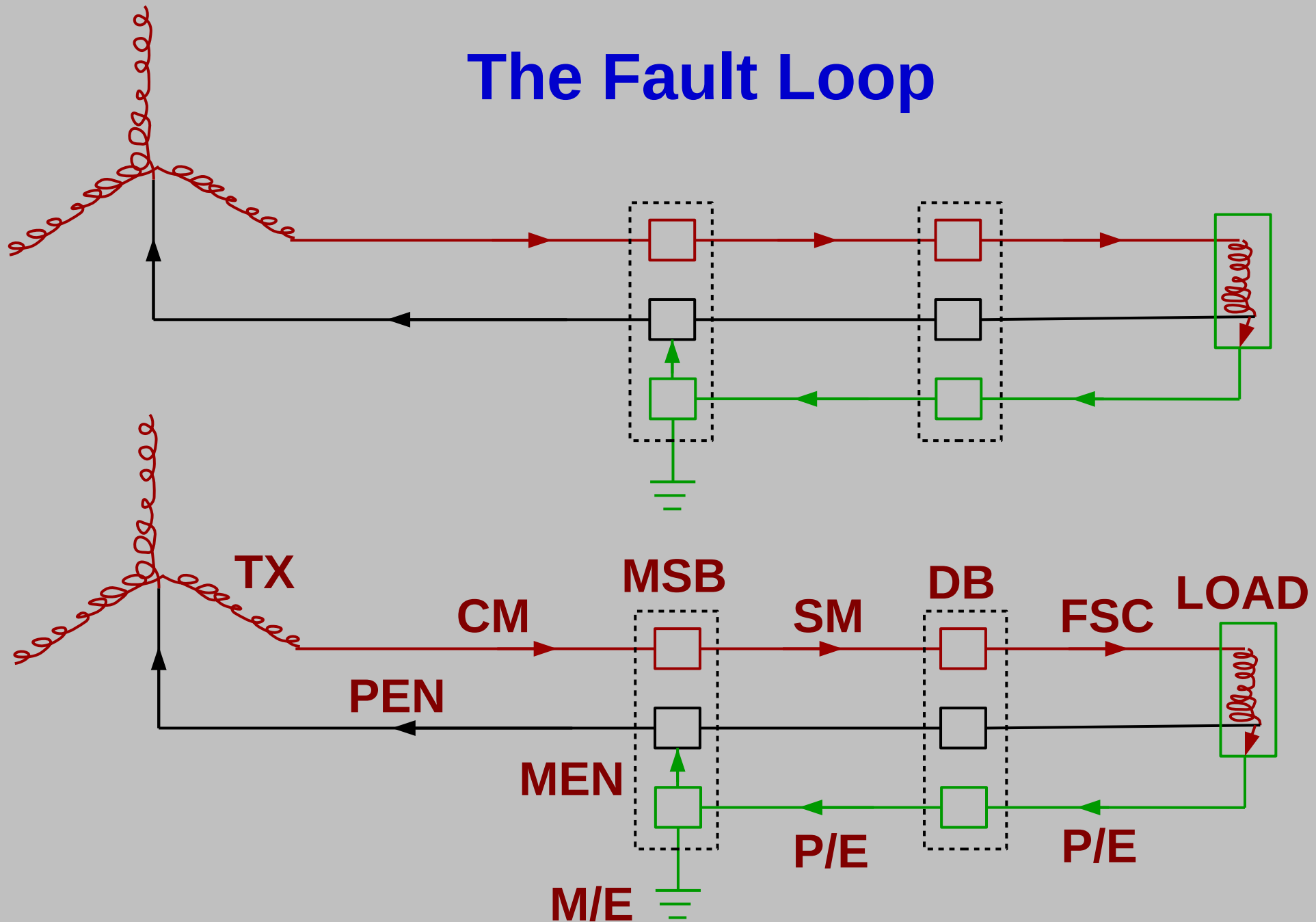


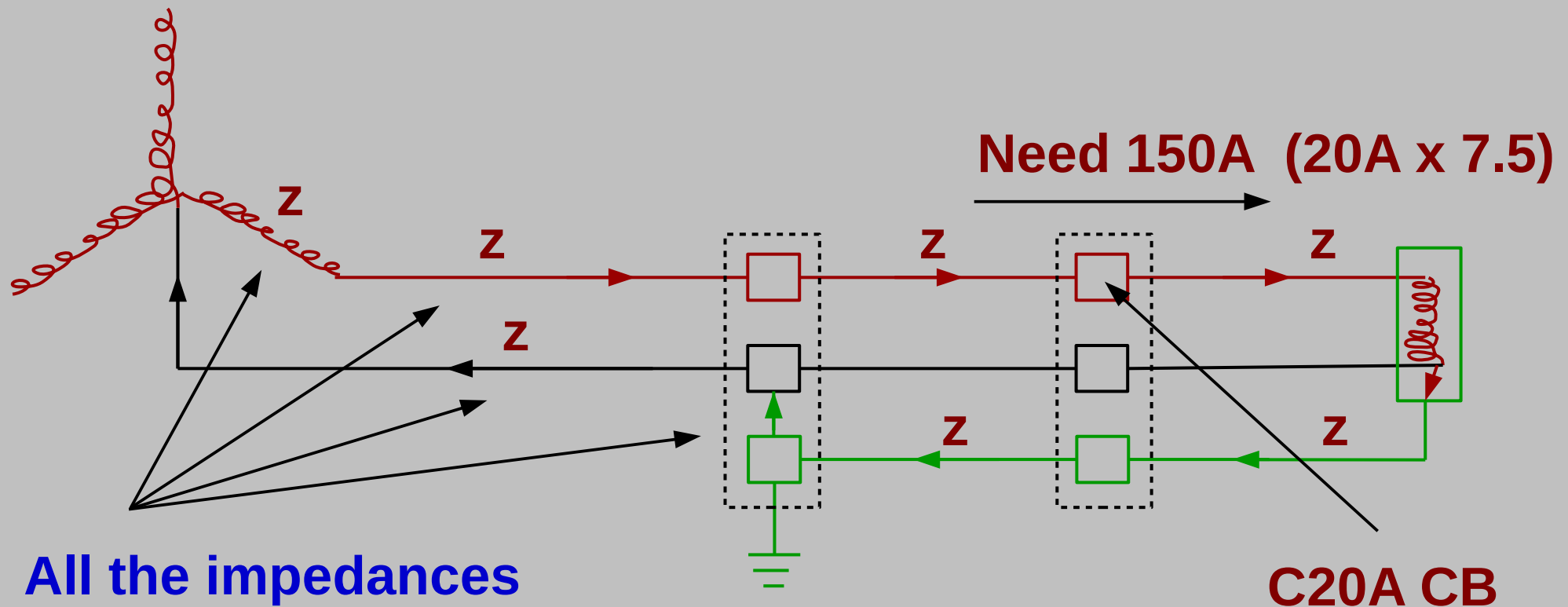

All the impedances added together makes the Fault-Loop Impedance

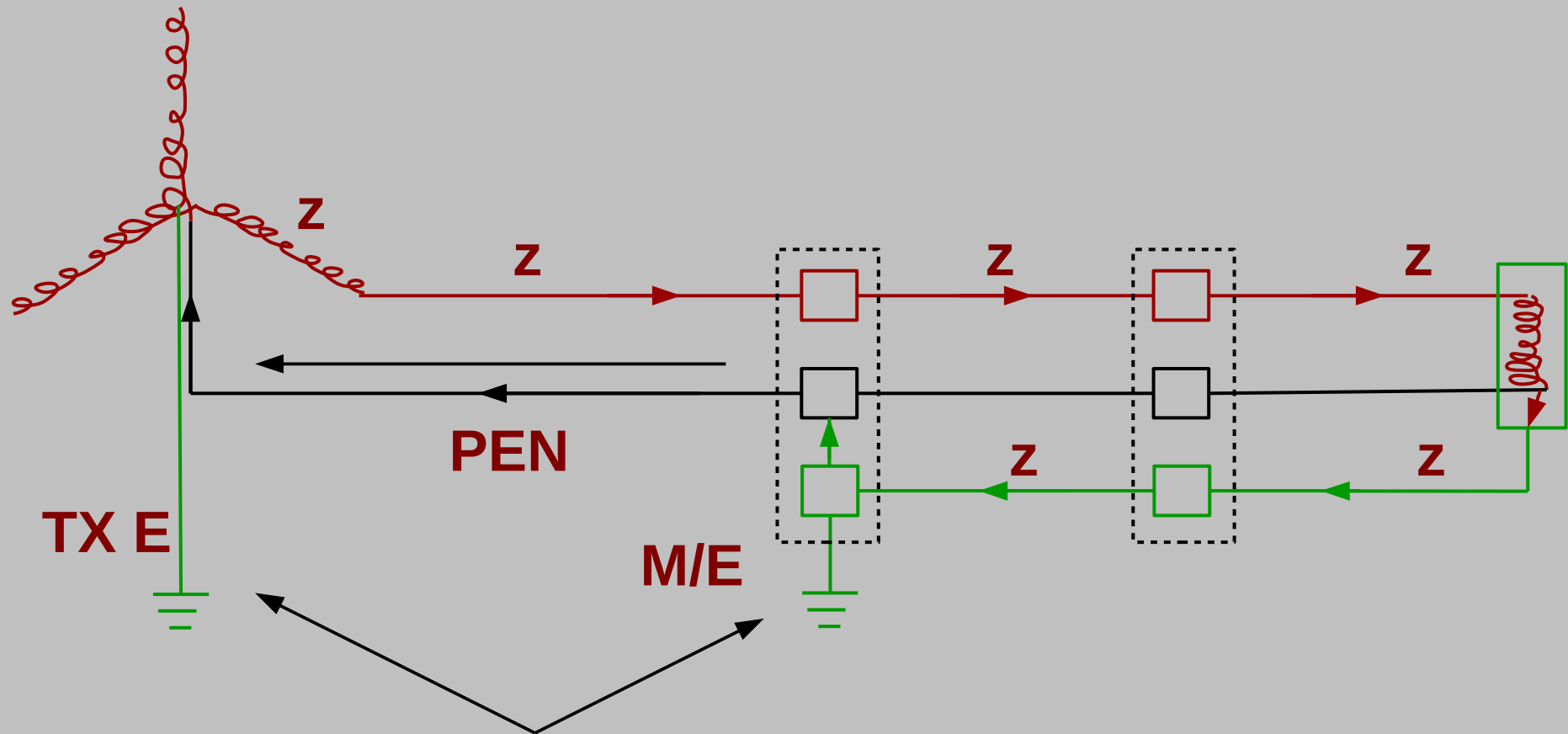
**5.7.4 AS/NZS 3000** gives the formula:  $Z_s \times I_a \leq U_o = Z_s = \frac{U_o}{I_a}$  or  $(Z_{max} = \frac{V}{I_a})$

$I_a$  – Is the current required to trip the circuit breaker. ( $I_a$  is Amps rated on the circuit breaker times the class)



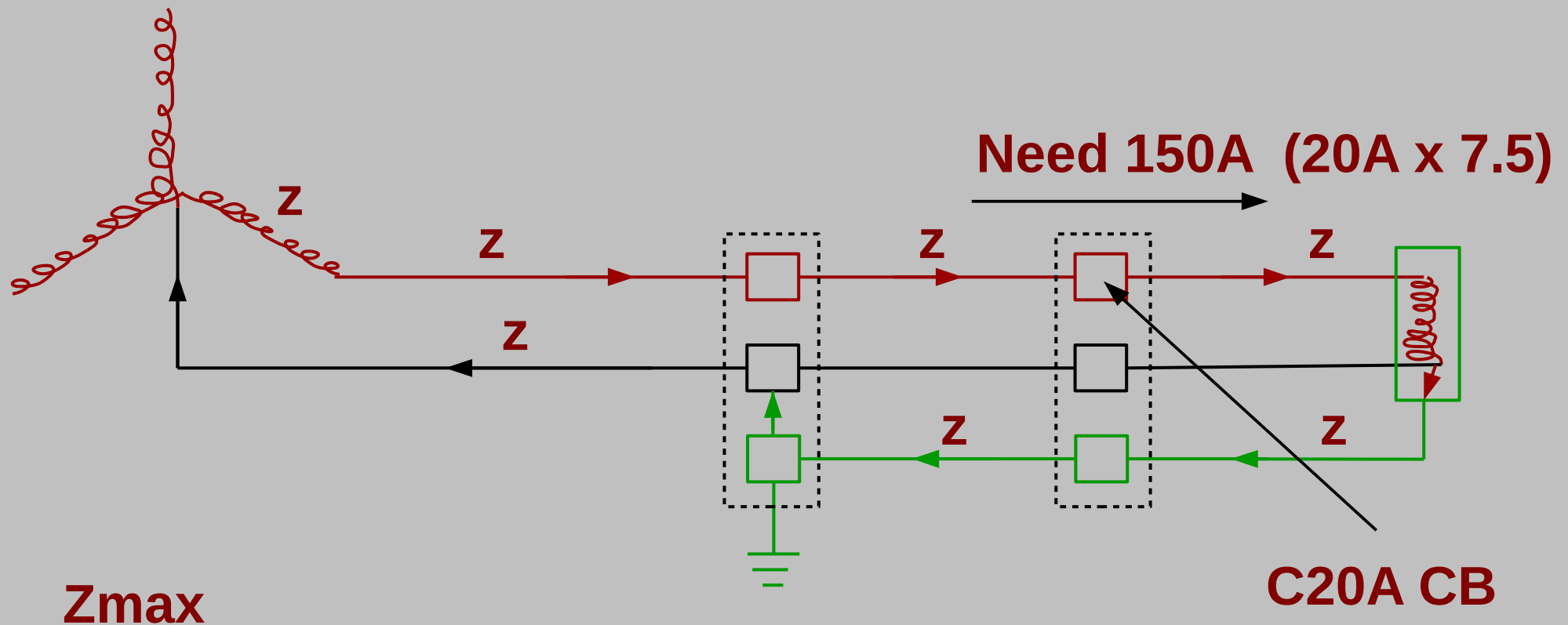
Barely any current runs through the ground as the impedance is much higher than the PEN conductor





$$Z_{\max} = \frac{V}{I_a} = \frac{230}{(7.5 \times 20)} = 1.533 \Omega$$

**Now check this against Table 8.1**

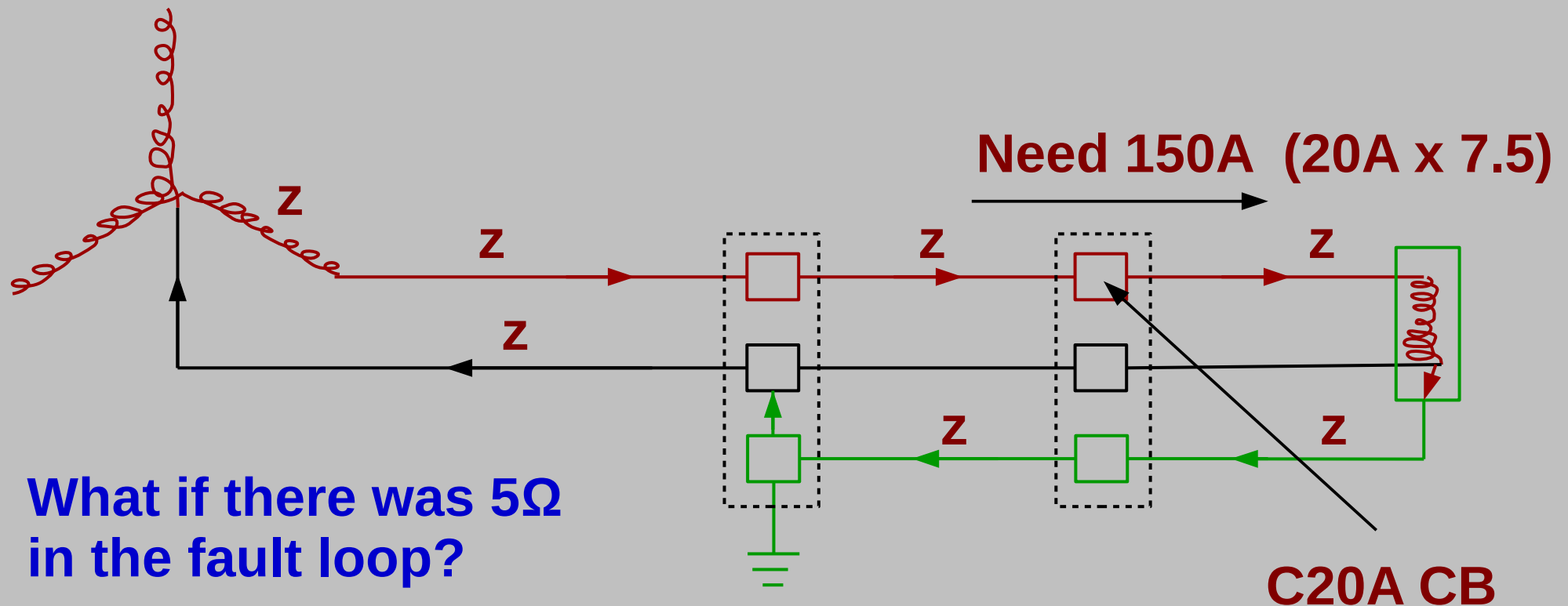


What if there was 5Ω  
in the fault loop?

Transposed = 
$$I_a = \frac{V}{Z} = \frac{230 \text{ V}}{5 \Omega} = 46 \text{ A}$$


$$\frac{46 \text{ A}}{20 \text{ A}} = 2.3 \times \text{Overload}$$

How long will it take to trip the CB

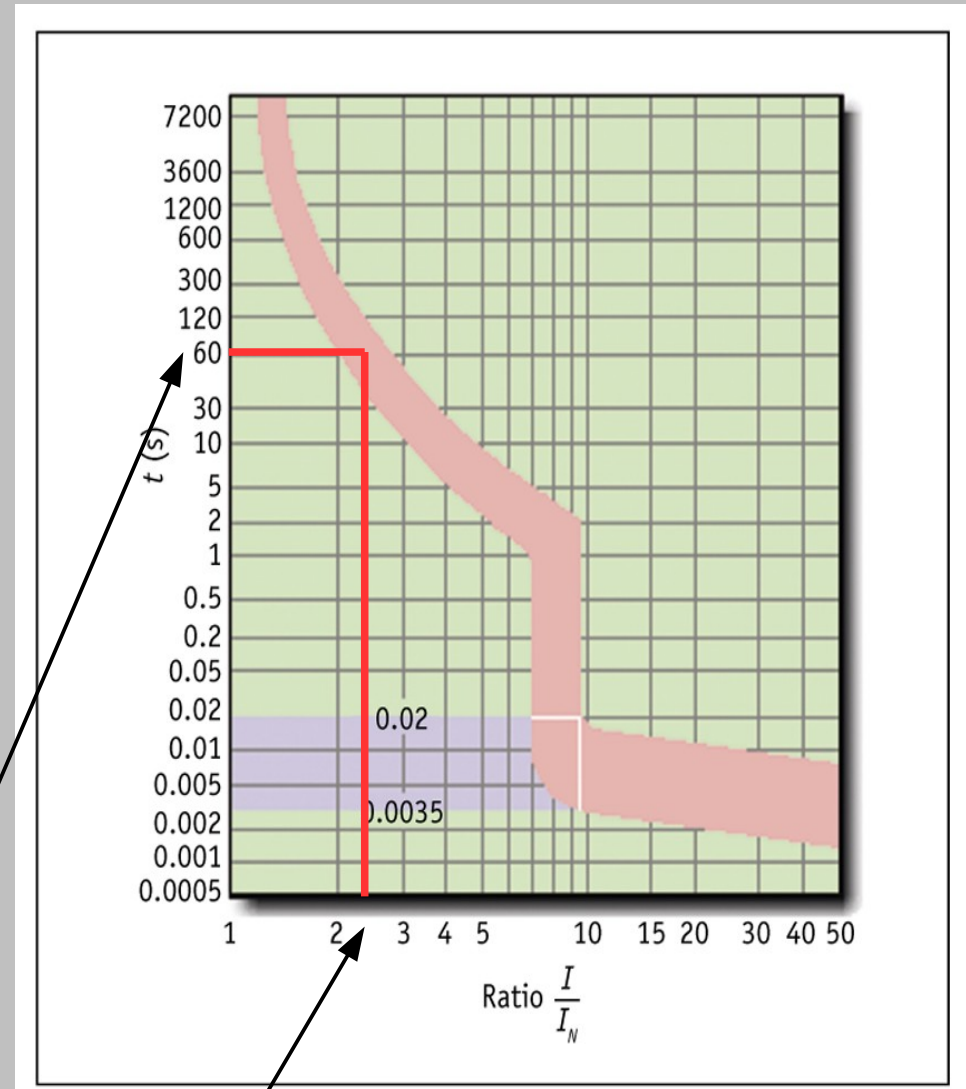Not fast enough (60 seconds) we need 7.5 x overload to turn the power off in 0.4 seconds max.  
5.7.2 AS/NZS 3000



2.3 x Overload

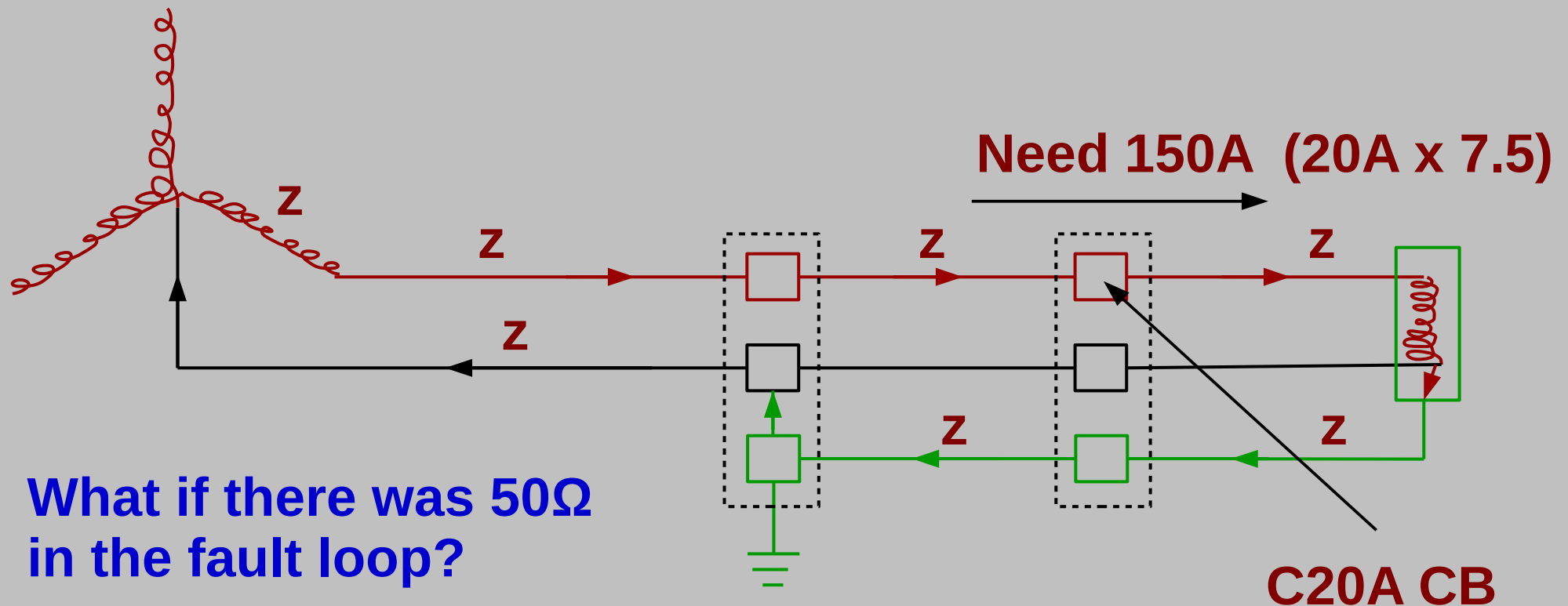


$$I_a = \frac{V}{Z} = \frac{230 \text{ V}}{50 \Omega} = 4.6 \text{ A}$$

4.6 A = 0 × Overload


How long will it take to trip the CB

**A circuit breaker may  
never trip with a 50Ω  
Fault-Loop**

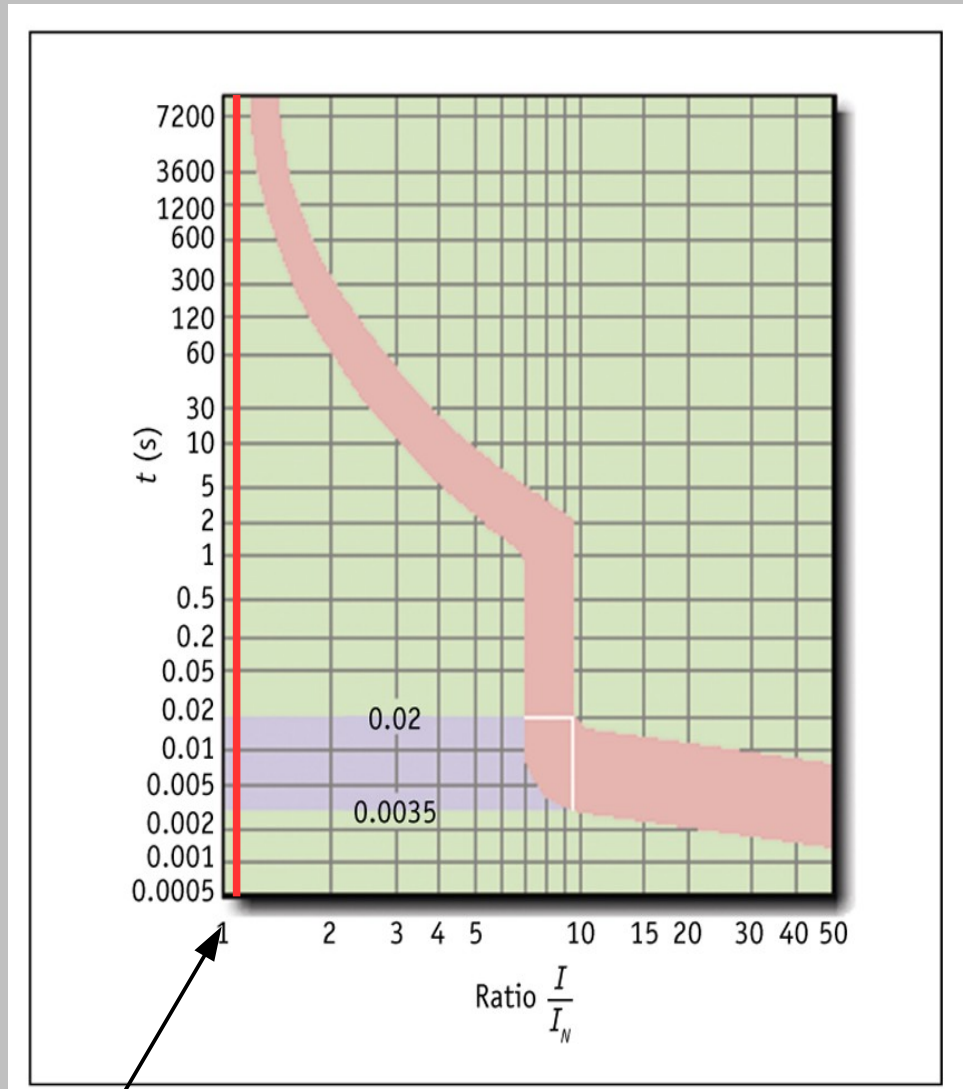**Don't leave the MEN out  
or you will render your  
circuit breakers  
useless!**



**0 x Overload**

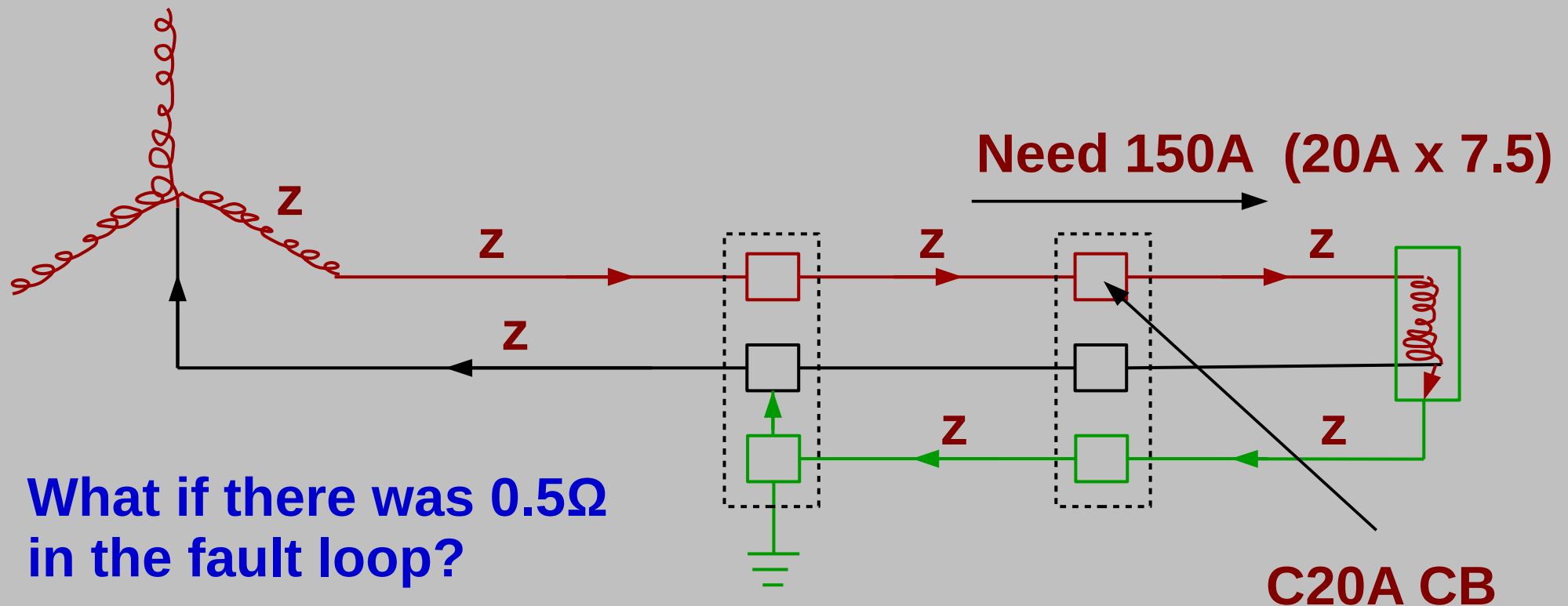


What if there was  $0.5\Omega$  in the fault loop?

$$I_a = \frac{V}{Z} = \frac{230 \text{ V}}{0.5 \Omega} = 460 \text{ A}$$

$$\frac{460 \text{ A}}{20 \text{ A}} = 23 \times \text{Overload}$$

How long will it take to trip the CB

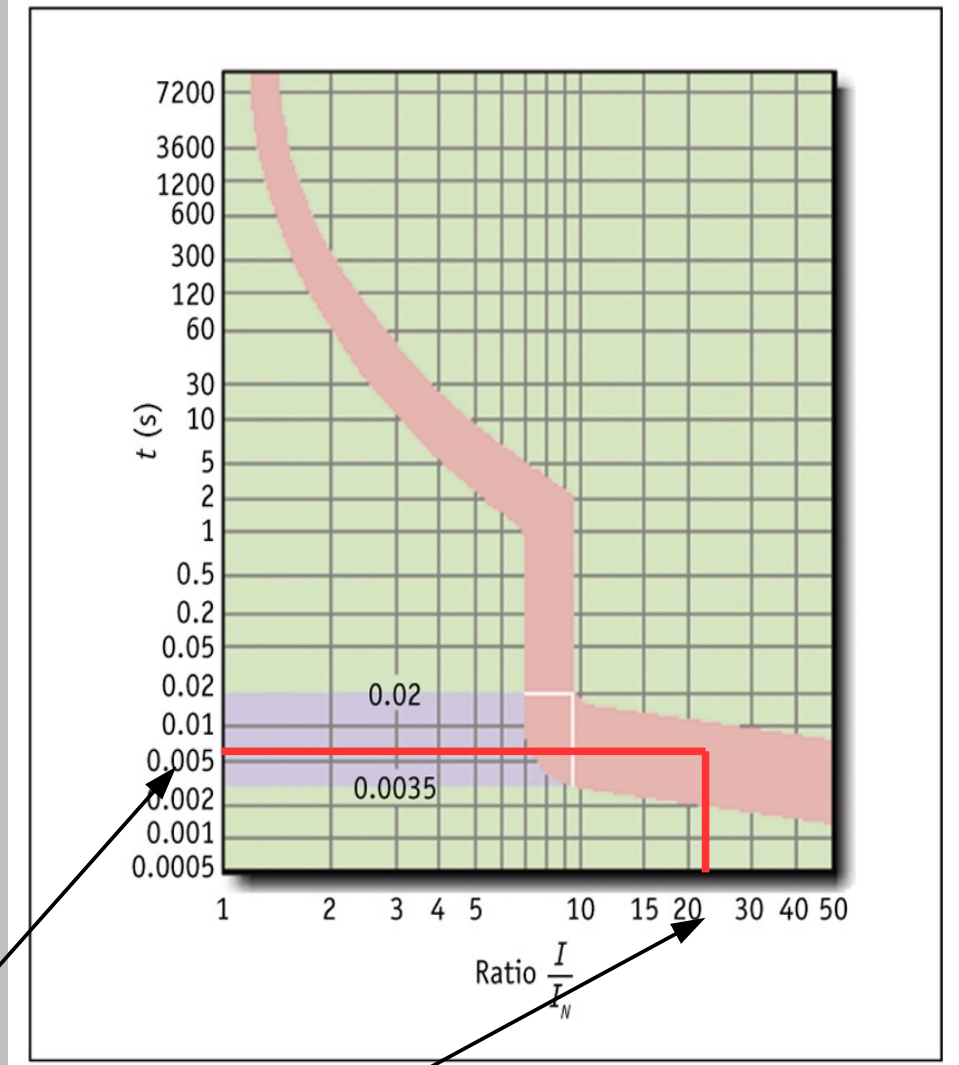
**Easily faster than the  
minimum disconnection  
time or 0.4 seconds**




**23 x Overload**

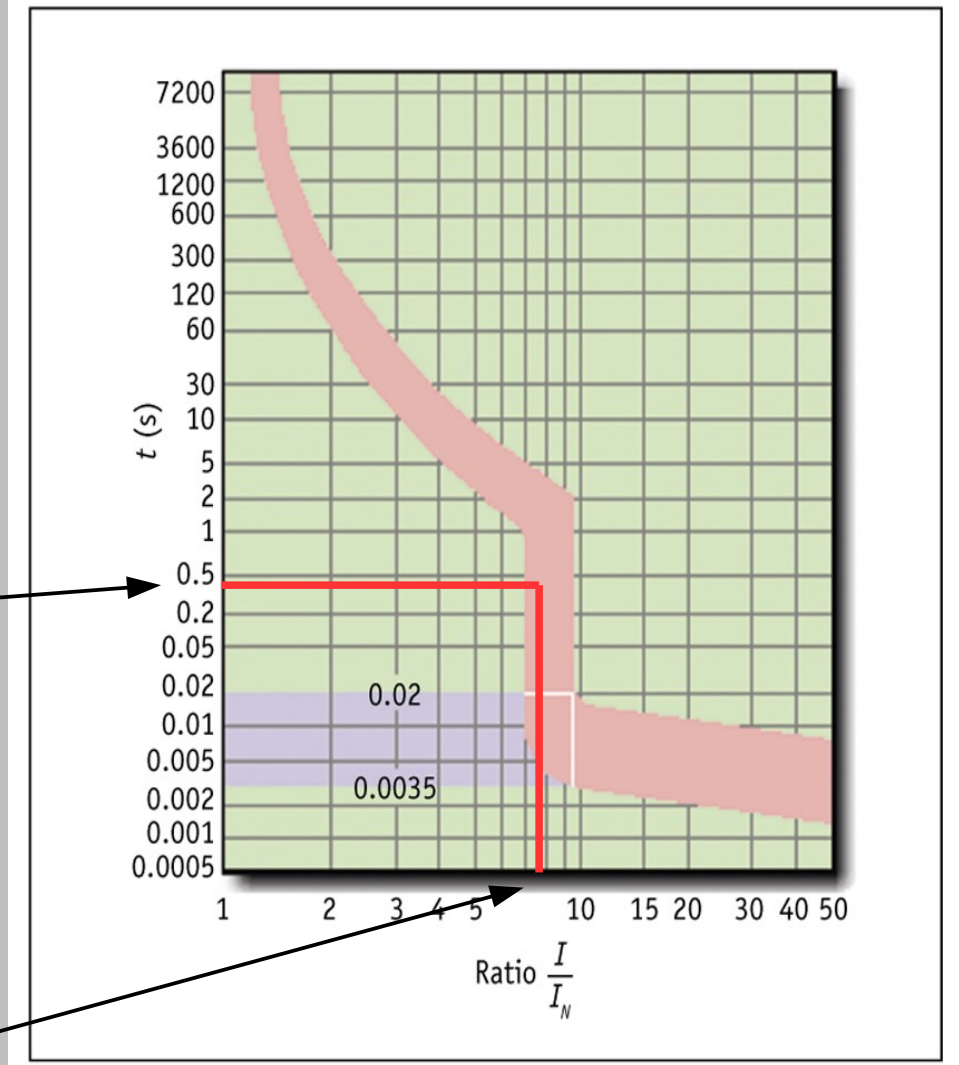7.5 x overload is the minimum current required to cause automatic disconnection of supply, (in 0.4 s) therefore  $1.53\Omega$  is the maximum fault-loop impedance for a C20A CB

$$Z_{\max} = \frac{V}{I_a} = \frac{230}{(7.5 \times 20)} = 1.533 \Omega$$





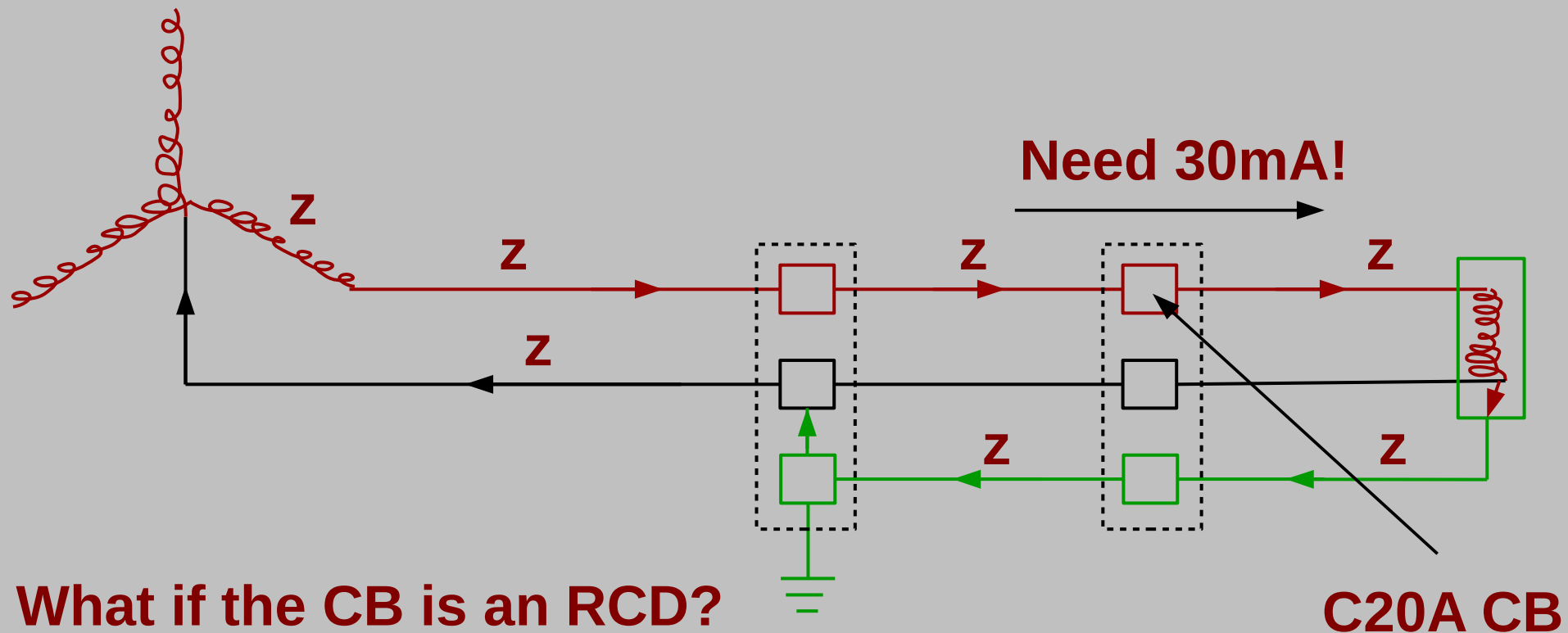


What if the CB is an RCD?

$$RCD = \frac{230 \text{ V}}{30 \text{ mA}} = 7667 \Omega$$

You can have almost 8kΩ in the fault loop and it will still trip (if the RCD is faulty, we are back to needing 150A)

## Live testing

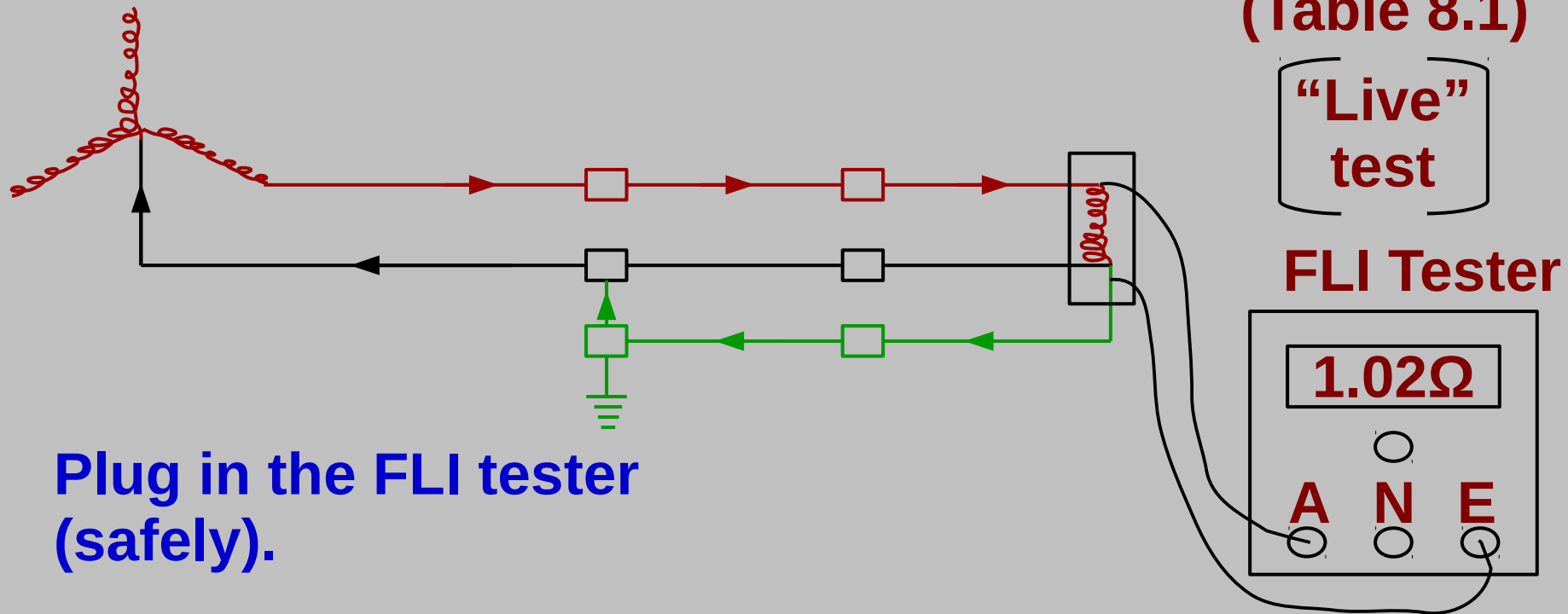


Plug in the FI tester  
(safely).

Press the test button.

The value must be less  
than those in table 8.1  
( $Z_{max}$  for live test)


## Dead testing

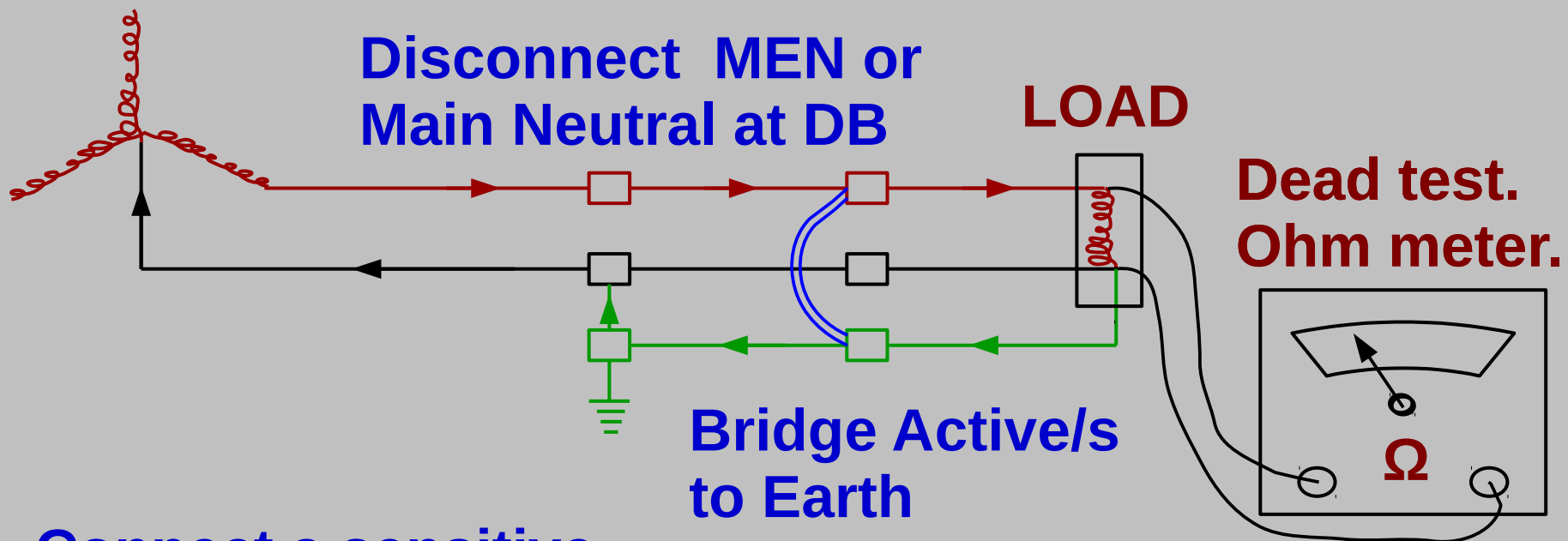

Connect a sensitive Ohm meter


The value must be less than those in table 8.2 (Zmax for dead test)

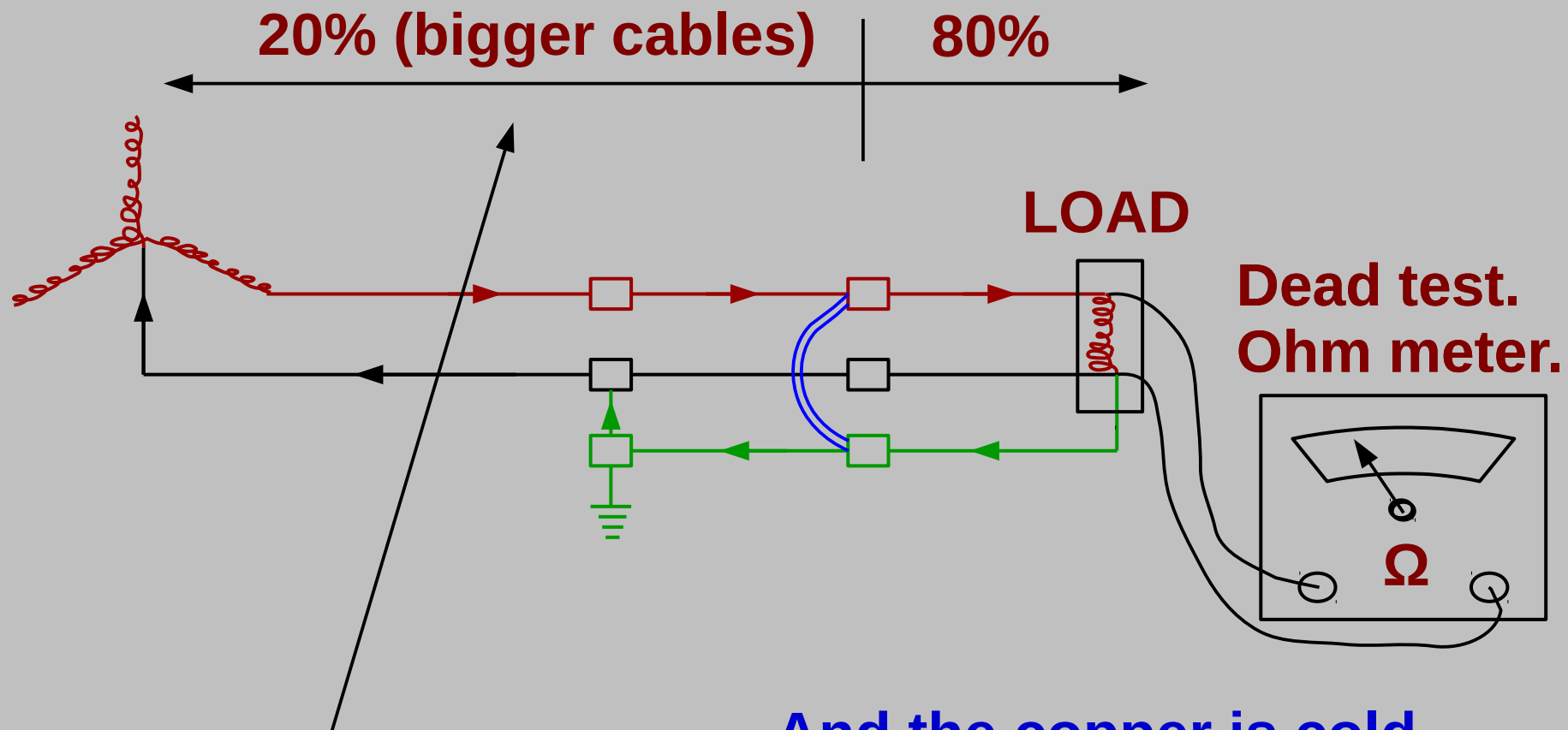A method accepted by AS/NZS 3000 that does not require an expensive meter



However this method  
does not test 20% of  
the circuit

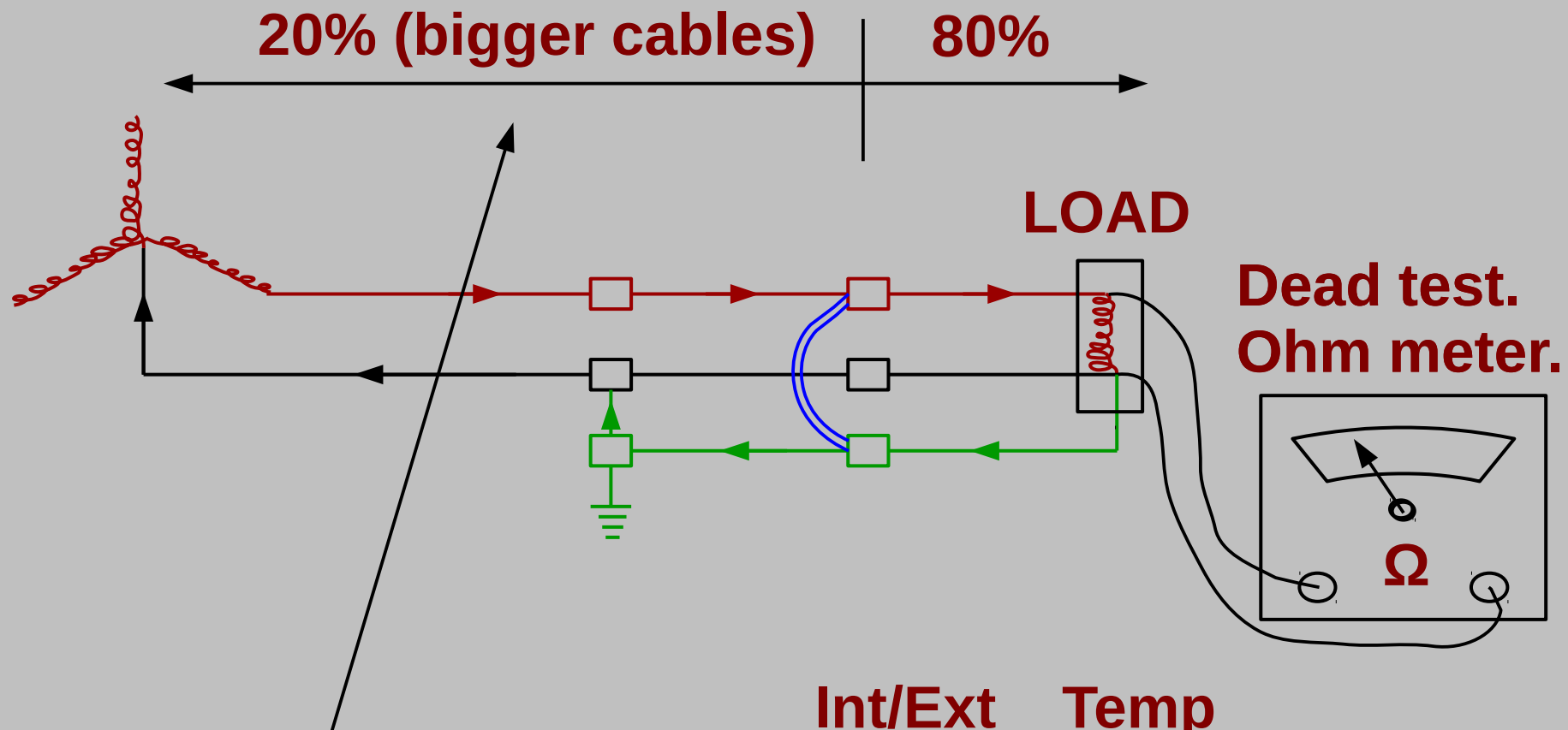And the copper is cold  
when tested and could  
have a higher resistance  
when operating at 75°



Therefore we use the following modified formula:

$$Z_{\max} = \frac{V}{I_a} \times \text{Int/Ext} \times \text{Temp}$$

$$0.8 \times 0.8 = 0.64$$

$$Z_{\max} = \frac{V}{I_a} \times 0.64 = \frac{230}{(20 \times 7.5)} = 0.98 \Omega$$

**Now check this against Table 8.2 ( $R_{\text{phe}}$ )  
(Resistance Phase to Earth)**

## Max Circuit length

(So as not to have FLI issues)

Lmax – Maximum length

B5.2.2 AS/NZS 3000

$$L_{\max} = \frac{0.8 \times U_o \times S_{\text{ph}} \times S_{\text{pe}}}{I_a \times \rho \times (S_{\text{ph}} + S_{\text{pe}})}$$

Use Table B1 for most cases

$U_o$  – Nominal phase volts (230V)

$S_{\text{ph}}$  – Cross section area of the active conductor in mm<sup>2</sup>

$S_{\text{pe}}$  – Cross section area of the protective Earthing in mm<sup>2</sup>

$I_a$  – Trip setting x Rating of Circuit Breaker (e.g. 20 x 7.5)

$\rho$  – Resistivity at normal working temperature in  $\Omega\text{-mm}^2/\text{m}$

Cu – 0.0225 $\Omega$

Al – 0.036 $\Omega$

**What is the max length of cable protected by a C20A CB with a 2.5mm Active and a 2.5mm Earth**


$$L_{\max} = \frac{0.8 \times U_o \times S_{\text{ph}} \times S_{\text{pe}}}{I_a \times \rho \times (S_{\text{ph}} + S_{\text{pe}})}$$

$$\begin{aligned} L_{\max} &= \frac{0.8 \times 230 \times 2.5 \times 2.5}{7.5 \times 20 \times 0.0225 \times 5} \\ &= \frac{1150}{16.875} \\ &= 68.15 \text{ metres} \end{aligned}$$


**Now check against table B1**



## Why are slabs bonded under wet areas?

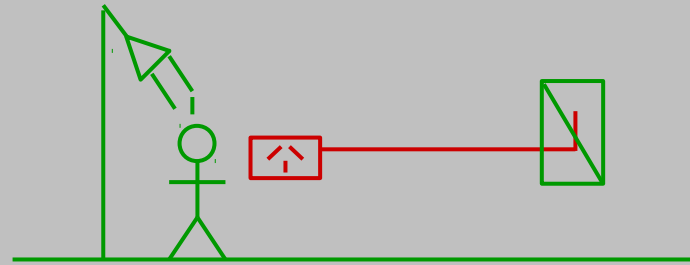

**No Earth?  $\Omega$ ?**

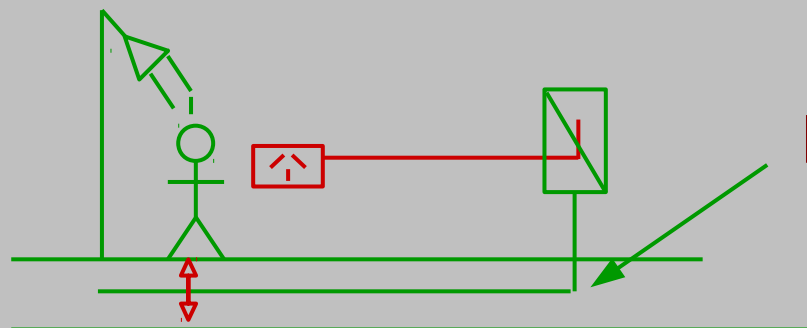

**Bonded Slab**

**FLI < much lower**